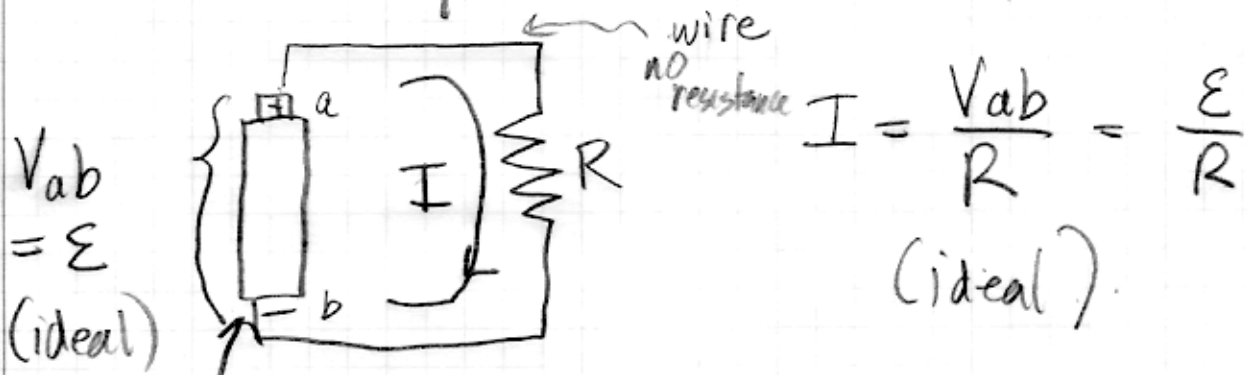





"Electromotive Force"

Force that moves charge in the "wrong" direction, that is, from low voltage to high voltage, is electromotive force.

⇒ battery is best example.



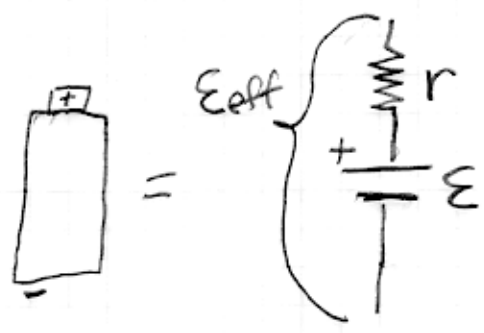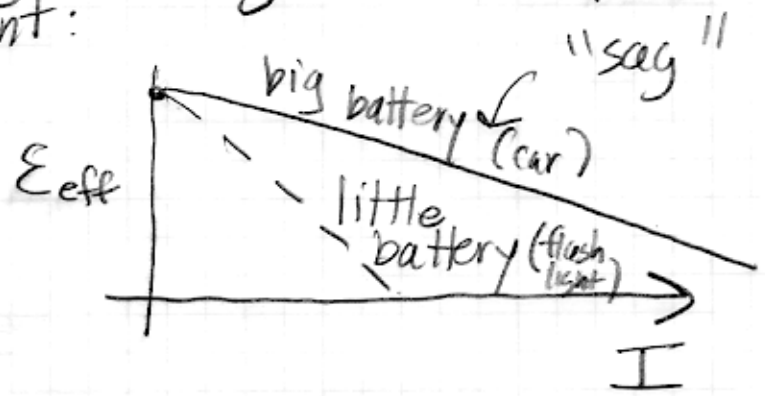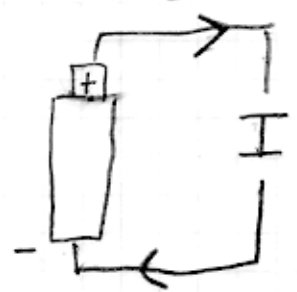Chemistry inside pushes charge back up to the higher potential
Battery voltage "sags" as it pumps out increasing current:




"internal resistance" makes


$$\epsilon_{eff} = \epsilon - Ir$$

$r =$ larger: littler battery
 $=$ smaller: bigger battery


Circuit Diagrams... symbols

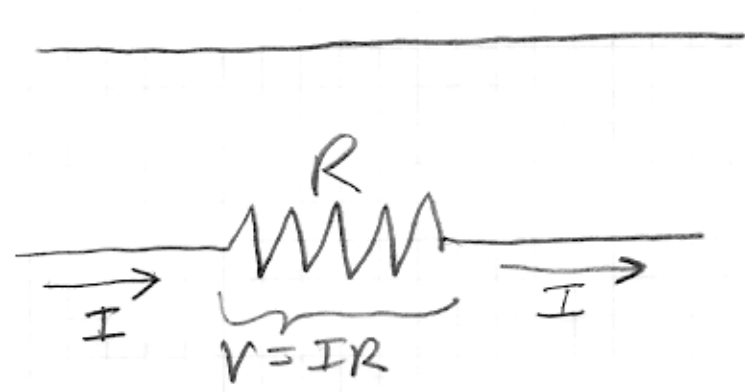

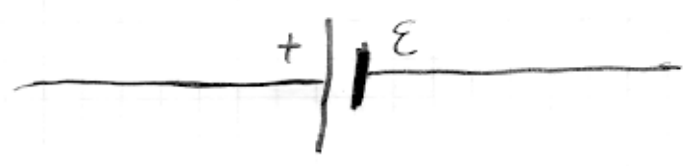
wire,
negligible
resistance
wires leading
to resistor




ideal "battery"

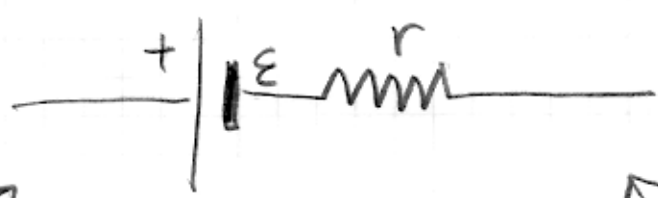

real batteries

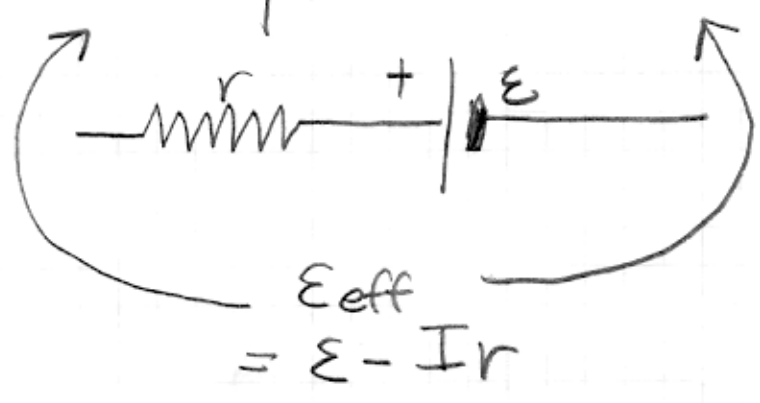

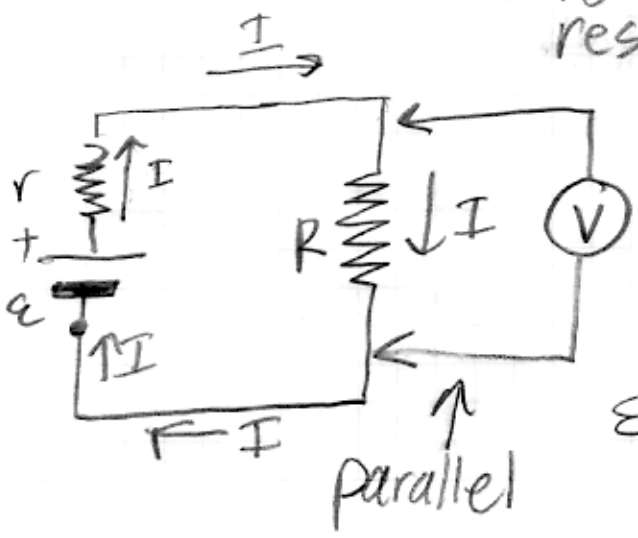
Voltmeters :
 • measure voltage
 • ideally, itself has infinite resistance
 • put in parallel



(Symbol)
 Volt meter, no current goes into it.
 measures here


$$\epsilon_{eff} = \epsilon - Ir, \quad = IR \Rightarrow I = \frac{\epsilon}{r+R}$$

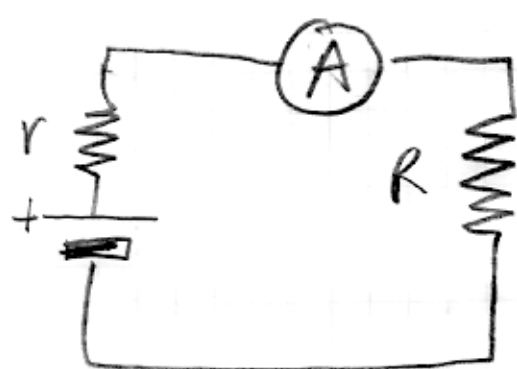- Ammeters :
- measure current
 - ideally, itself has 0 resistance
 - put in series




← no new resistance.
allows measurement of current



Nice Visualization :

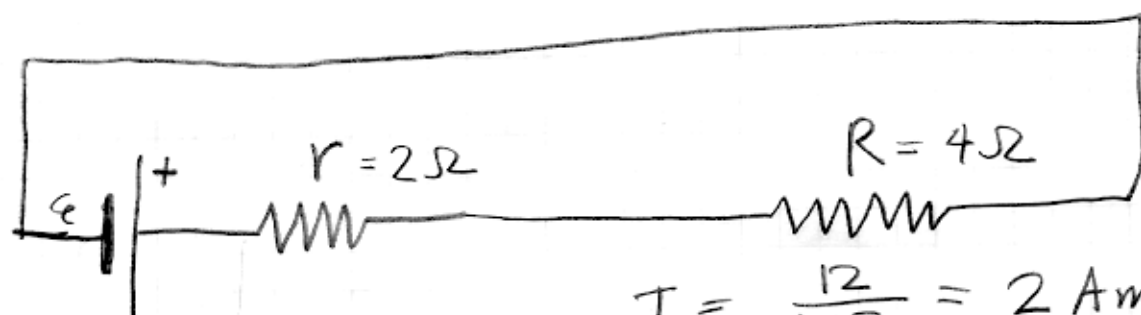

$$I = \frac{12}{4+2} = 2 \text{ Amps}$$

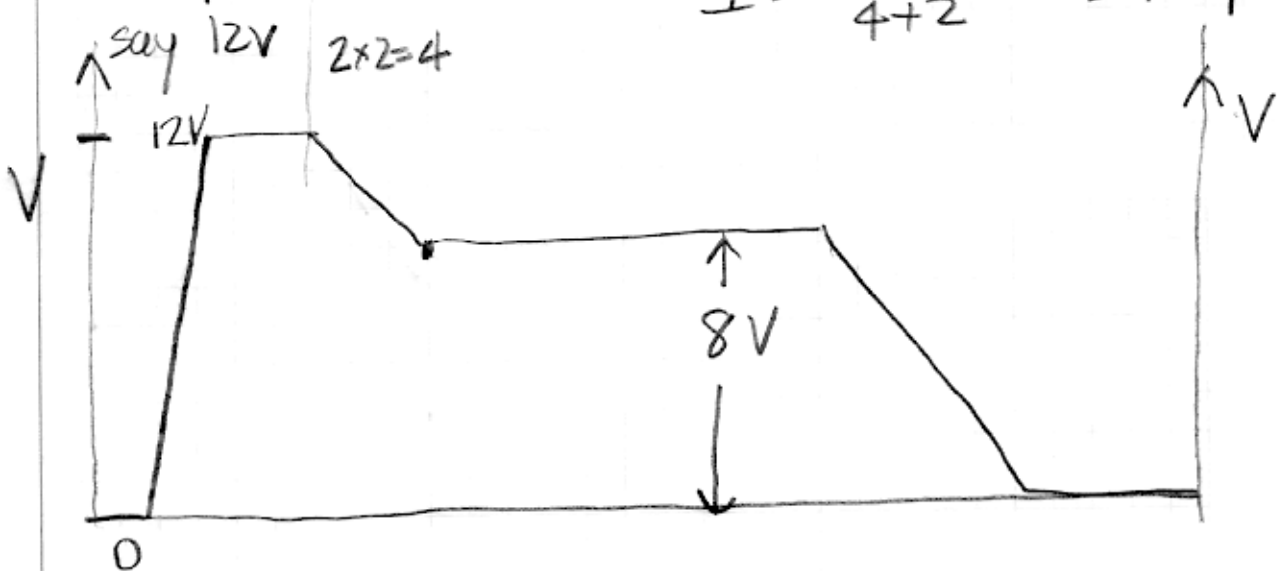

Energy & Power

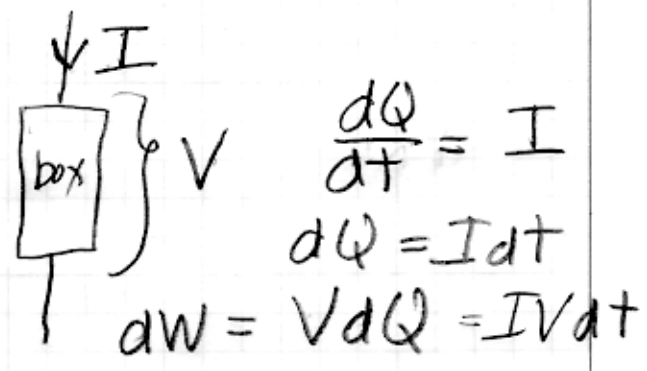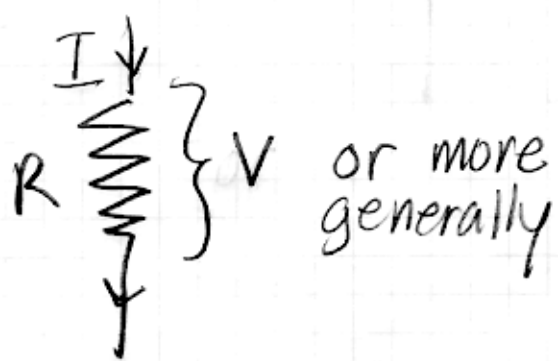

$$\text{power} = \frac{dW}{dt} = IV \quad (\text{important})$$

Resistor: $V = IR$

$$P = I^2 R = \frac{V^2}{R}$$

Problem 26-59

<u>Wire Gauge</u>	<u>diameter (cm)</u>	<u>$I_{\max} (A)$</u>	<u>$\left(\frac{I^2}{d^3}\right)$</u>
14	0.163	18	≈ 1
10	0.259	30	0.69
8	0.326	40	0.62
6	0.412	60	0.69
4	0.519	85	0.69

(a) look at power

$$I^2 R \propto R = \rho \cdot \frac{L}{A} = \rho \cdot \frac{L}{\pi r^2} = \frac{4\rho}{\pi} \frac{L}{d^2}$$

this will heat wire; wire will cool too, in proportion to the area of the outer surface of the wire, $A_{\text{outer}} = (2\pi r) \cdot L = \pi d \cdot L$


$$\frac{\text{Power}}{\text{outer area}} = \frac{I^2 R}{A_{\text{outer}}} = \frac{4\rho L}{\pi d^2} \frac{I^2}{\pi d L}$$

$$\frac{\text{Power}}{\text{outer area}} = \frac{4\rho}{\pi^2} \cdot \frac{I^2}{d^3}$$

$$\frac{I^2}{d^3} \Rightarrow \text{wire gauge } \left(\frac{I^2}{d^3} \right)_{14} = \frac{18^2}{0.163^3} = 74814 \frac{\text{A}^2}{\text{cm}^3}$$

others, normalize to this value:

$$\frac{\left(\frac{I^2}{d^3} \right)_{10}}{\left(\frac{I^2}{d^3} \right)_{14}} = \frac{51802}{74814} = 0.69$$

(b)  Incoming Current



$$4200 \text{ Watts} = IV$$

$$I = \frac{4200}{120} = 35 \text{ A}$$

Gauge 8-wire

$$(c) L = 42 \text{ m}$$

$$R = \frac{\rho \cdot L}{A} = \frac{\rho \cdot L}{\pi (D/2)^2}$$

$$= (1.7 \cdot 10^{-8} \Omega \cdot \text{m}) \cdot \frac{42 \text{ m}}{\pi \left(\frac{0.326 \cdot 10^{-2} \text{ m}}{2} \right)^2}$$

$$R = 8.6 \cdot 10^{-2} \Omega$$

$$P = I^2 \cdot R = 35^2 \cdot 8.6 \cdot 10^{-2} = 106 \text{ Watts}$$

(d) two ways: (i) compute R'

$$R' = \frac{\rho \cdot L}{\pi (D'/2)^2} = 5.4 \cdot 10^{-2} \Omega$$

$$P' = I^2 \cdot R' = 35^2 \cdot 5.4 \cdot 10^{-2} = 66 \text{ Watts}$$

$$(ii) \frac{P'}{P} = \left(\frac{D}{D'} \right)^2 = \left(\frac{0.326}{0.412} \right)^2 = 0.626$$

$$P' = 0.626 \cdot P = 0.626 \times 106 = 66 \text{ Watts}$$


$$\Delta E = \Delta P \cdot t = (P - P') \cdot t$$

$$t = 12 \frac{\text{hours}}{\text{day}} \cdot 365 \frac{\text{days}}{\text{year}} = 4380 \frac{\text{hours}}{\text{year}}$$

$$\Delta E = \frac{(106 - 66) \cdot 4380}{1000} \text{ kw-h} = 172 \text{ kw-h}$$

$$\$ = \Delta E \cdot (\text{Price/kwh}) = 172 \cdot 0.11 = \$18.8$$

26-61

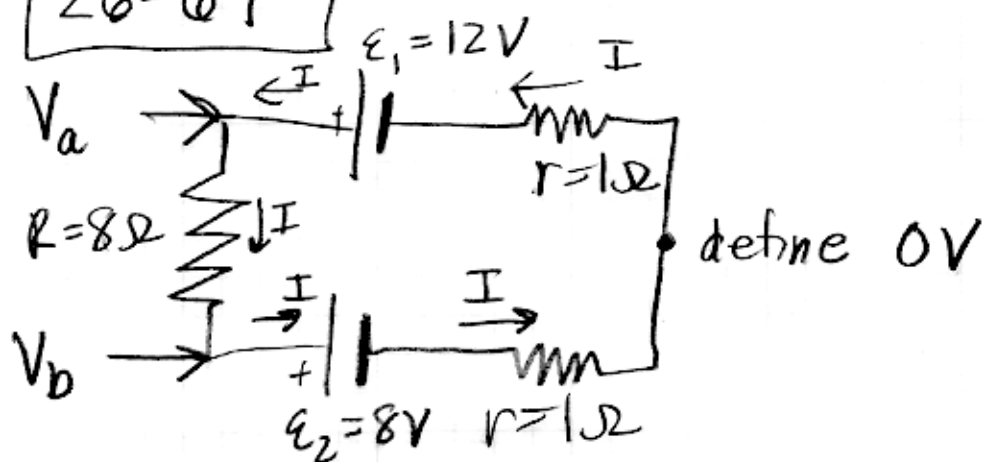

$$(a) \quad V_a = -r \cdot I + \epsilon_1$$

$$V_b = +r \cdot I + \epsilon_2$$

$$I = \frac{V_a - V_b}{R} = \frac{-rI + \epsilon_1 - rI - \epsilon_2}{R}$$

$$\left(1 + 2\frac{r}{R}\right) I = \frac{\epsilon_1 - \epsilon_2}{R}$$

$$I = \frac{\epsilon_1 - \epsilon_2}{R\left(1 + \frac{2r}{R}\right)} = \frac{\epsilon_1 - \epsilon_2}{R + 2r}$$

$$I = \frac{12 - 8}{8 + 2 \cdot 1} = \frac{4}{10} = 0.4 \text{ A}$$

$$(b) \quad P_R = I^2 \cdot R = 0.4^2 \cdot 8 = 1.28 \text{ W}$$

$$P_{\text{batt}} = I^2 \cdot r = 0.4^2 \cdot 1 = 0.16 \text{ W} \quad (2 \text{ of these})$$

$$\text{Total dissipation} = 1.28 + 2 \cdot 0.16 \\ = 1.6 \text{ W}$$

(c) #1 pumps wt, $P_1 = I \varepsilon_1$
 (big voltage)
 $= 0,4 \cdot 12 = 4,8 \text{ W}$

(d) #2 gets pumped up, $P_2 = -I \varepsilon_2$
 $= -0,4 \cdot 8 = -3,2 \text{ W}$

(e) (#1 wt) = 4,8 W

(#2) = -3,2 W (- "lost")

dissipation = -1,6 W (- "lost")

0 W energy conserved