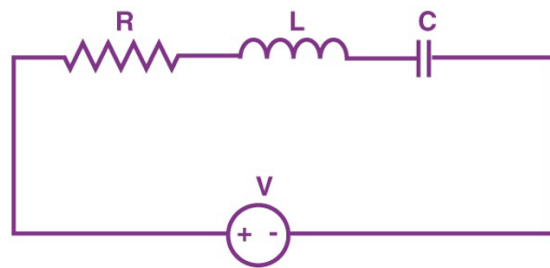



# How to use Kirchoff's voltage law in a circuit

Claudio C.

I have fielded a few questions on how to get all the signs right when applying Kirchoff's law to a circuit that includes batteries, capacitors, resistors, and inductors. It is indeed easy to get the signs wrong. My advice is to be **very** pedantic, label everything in sight, and do not skip steps. For example, consider the circuit below.



Here is how I would label it

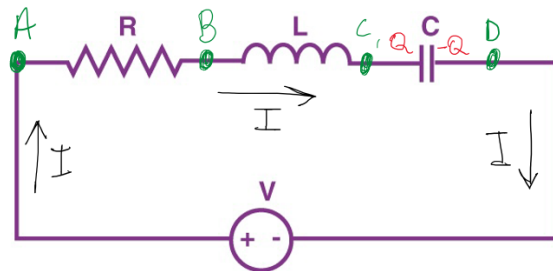

Let's review what I did

- I labelled all nodes in the circuit ( $A, B, C, D$ ).
- I picked a sign convention for the current  $I$ : positive current is defined as flowing in the clockwise direction. This choice is entirely arbitrary.
- I picked a sign convention for charge  $Q$ . With this convention  $Q(t) > 0$  at any given time  $t$  means that at time  $= t$  there is positive charge on the left side of the capacitor and  $Q(t) < 0$  means the opposite. This choice is also entirely arbitrary.

Next I have to figure out the relationship between  $I$  and  $Q$ . Is it  $I = +dQ/dt$  or  $I = -dQ/dt$ ? With my convention, if  $I$  is positive then positive charge flows on the left side of the capacitor, so with my sign convention for  $Q$ ,  $dQ/dt$  is also positive. Thus  $I = +dQ/dt$ .

Kirchoff's law is  $(V_A - V_B) + (V_B - V_C) + (V_C - V_D) + (V_D - V_A) = 0$ . This is not a fancy law, it is just elementary-school algebra (**but see the comment at the end!**). Now we have to figure out all the  $(V_i - V_j)$ 's one-by-one and get the signs right. Here it goes:

- $V_A - V_B = +IR$ . Why? Because current in a resistor flows from the more positive end to the less positive end. With our convention if  $I > 0$  current flows from  $A$  to  $B$ , and so  $V_A > V_B$  if  $I > 0$ . Therefore I need a plus sign.
- $V_C - V_D = +Q/C$ . Why? Because when positive charge is on one side of a capacitor then that side is at the higher voltage. With my charge convention for  $Q$ , when  $Q$  is positive  $V_C > V_D$ . So a plus sign.
- $V_D - V_A = -V$ . Why? Here I am interpreting the circuit diagram notation as telling me that when  $V$  is positive the left side of the battery (or the AC generator) is more positive than the right side. The left side is node  $A$ , the right side is node  $D$ , so when  $V$  is positive  $V_A > V_D$ . So a negative sign.
- $V_B - V_C$  is the trickiest. Is it  $+LdI/dt$  or  $-LdI/dt$ ? Realize that  $V_B - V_C$  is an emf so think of it as sticking a battery in the circuit instead of having the inductor. This battery (emf) wants to drive a current that opposes the change in  $I$ . So if  $dI/dt$  is positive, *i.e.*, if  $I$  increases in the clockwise direction, then this battery (emf) would drive current in the anticlockwise direction. A battery between nodes  $B$  and  $C$  would drive current in the anticlockwise direction if  $V_B > V_C$ . Thus  $V_B - V_C = +LdI/dt$ .

Putting it all together Kirchoff's law becomes

$$IR + L\frac{dI}{dt} + \frac{Q}{C} - V = 0$$

$$R\frac{dQ}{dt} + L\frac{d^2Q}{dt^2} + \frac{Q}{C} = V$$

Now, to be perfectly honest, I cheated a little bit. Kirchoff's law for voltages is based on the assumption that  $\oint \mathbf{E} \cdot d\mathbf{l} = 0$ . This does not apply if they are changing magnetic fields. But in an inductor, if the current changes, *i.e.*,  $\frac{dI}{dt} \neq 0$  the assumption fails. This is discussed in these two nice videos from Rice University. Take a few minutes to watch them

1. [https://www.youtube.com/watch?v=ld6d\\_nRTI4](https://www.youtube.com/watch?v=ld6d_nRTI4)
2. <https://www.youtube.com/watch?v=UNmEayHrCJg>