Fall 2004 Physics 3 Tu-Th Section

Claudio Campagnari Lecture 15: 18 Nov. 2004

Web page: http://hep.ucsb.edu/people/claudio/ph3-04/

Last Time: Electrical Current

• Electrical Current = measure of the flow of charge

- Defined in terms of flow of positive charge
	- \triangleright even if in most case moving charges are electrons

• Measured in Coulomb/sec = Ampere (A) 2

Last Time: Drift Velocity

- In a conductor the free electrons are moving very fast in random directions ($v \sim 10^6$ m/sec)
- They collide with the atoms of the lattice and are scattered in random directions

- If an electric field is present, there is a slow net drift of electrons in the direction opposite the electric field
- $V_{DRIFT} \sim$ mm/sec

Last Time: Current & Current Density Ohm's Law

• $I = n q v_d A$

 \triangleright n = number of free charge carriers/unit volume

- Current density $J = I/A$
- Ohm's Law: $E = \rho J$
	- \triangleright ρ = resistivity

 $\triangleright \sigma = 1/\rho =$ conductivity

- \triangleright Good conductor: low ρ / high σ
- Ohm's Law: $I = \frac{V}{B}$
	- \triangleright R = resistance
	- \triangleright Measured in Volt/Ampere = Ohm (Ω)

4

• Consider a piece of wire with E-field....

• ...current flows, charge builds-up at ends...

• ...until the electric field from the build up of charge cancels the original electric field....

- ...and the current stops!
- To keep the current going, I need to somehow move the charges around a loop

Analogy: Water Fountain

High Potential

Low Potential

- Water moves from high potential energy to low potential energy
- Just like +ve charge moves from high electric potential to low electric potential
- To keep the water circulating, the water needs to be brought back to the top
- This process costs energy (work needs to be done)
- In a fountain the work is done by a pump

Electromotive Force

- In a electric circuit the "something" that makes charge move from low potential to high potential is called electromotive force (emf)
- It is not a mechanical force, the term is a bit confusing
- The device that provides the emf is called the "source of emf"
	- \triangleright e.g. a battery
	- \triangleright moral equivalent of the pump in a fountain

7

Source of emf

- An ideal source of emf is a device that maintains a constant potential difference across its terminals
- V_{ab} constant

$$
\begin{array}{c|c}\n\hline\na \\
+ \\
\hline\n\end{array}
$$

• When connected to an external circuit, the positive charges move in the circuit from the $+$ to the $$ terminal. When they reach the – terminal the emf is able to move them back, internally, to the + terminal

Ideal source of emf (continued)

• The emf (ϵ) is defined as the energy expended by the source to move unit charge from $b\rightarrow a$

Real source of emf

- In reality the source of emf needs to overcome
	- \triangleright Potential difference V_{ab} (ideal and real source)
	- \triangleright Some small resistance to current flow within the battery (real sources)
		- Internal resistance r
- If current I moves through the source, there will be an associated drop of potentaial $V=Ir$

$$
\bullet \ \mathsf{V}_{ab} = \varepsilon \cdot \mathsf{Ir}
$$

Circuit diagram symbols

Table 25.4 Symbols for Circuit Diagrams

Resistor

Conductor with negligible resistance.

Source of emf (longer vertical line always represent the positive terminal, usually the terminal with higher potential)

Source of emf with internal resistance $r(r \text{ can be placed on either})$ side)

Voltmeter (measures potential difference between its terminals)

Ammeter (measures current through it)

Ideal source of emf connected to resistor

Real source of emf connected to resistor

Example: Problem 25.35

- Switch open: $V_{open} = 3.08$ V
- Switch closed: V_{closed} =2.97 V, I=1.65 A
- Find emf, r, R

- Switch open:
	- \triangleright no current flows
	- $\geq \epsilon = V_{open} = 3.08$ V
- Switch closed:

 \triangleright V_{closed} = **ε** - Ir \rightarrow r = (**ε** – V_{closed})/I = (3.08 – 2.97)/1.65 = 0.067 Ω

 \triangleright \triangleright \triangleright \triangleright \triangleright \square $(R+r)$ \rightarrow $R = \frac{\mathcal{E}}{1 - r} = (3.08/1.65 - 0.067) \Omega = 1.8 \Omega$

 \triangleright OR: Voltage across R is V_{closed} \rightarrow R = V_{closed}/I = 2.97/1.65 = 1.8 Ω

Example: Problem 25.64

- 1. Label resistances, emfs, and intermediate points
- 2. Define direction of current (arbitrary)
- 3. Go around the circuit
	- $V_e V_b = I R_1$
	- $V_b V_a = IR_2$
	- $V_a V_f = I R_3$
	- $V_f V_g = I R_4$ • $V_q - V_d = \varepsilon_2$

$$
\mathsf{V}_{\mathsf{c}}
$$

$$
V_{d} - V_{c} = I R_{g}
$$

$$
V_{c} - V_{e} = -\varepsilon_{1}
$$

 $V_e - V_h = I R_1$ $V_b - V_a = I R_2$ $V_a - V_f = I R_3$ $V_f - V_g = I R_4$ $V_q - V_d = \varepsilon_2$ $V_{d} - V_{c} = I R_{5}$ $V_c - V_e = -\epsilon_1$

Clearly, I want to know the current I.

Sum up the 7 equations.

The left hand side is zero. This is no accident! I went around the loop and calculated potential drops. The total drop around the loop is zero.

0 = IR¹ + IR² + IR³ + ε² + IR⁵ - ε¹ 0 = IRtot + ε² - ε¹ (where Rtot is the sum of all resistances, Rtot = 32 Ω) I = (ε¹ - ε²)/Rtot = (4-8)/32 A = -1/8 A

16 $V_{ad} = V_a - V_d = (V_a - V_f) + (V_f - V_g) + (V_g - V_d) = I R_3 + I R_4 + \varepsilon_2$ $V_{ad} = (-1/8)8 \text{ V} + (-1/8)(1/2) \text{ V} + 8 \text{ V} = -1 \text{ V} - 1/16 \text{ V} + 8 \text{ V} = 6.94 \text{ V}$

Energy

- Consider circuit element
- Charge q moves $a \rightarrow b$
- Change in potential energy qV_{ab}
	- $\triangleright \Delta U = U_{\text{final}} U_{\text{initial}} = -qV_{\text{ab}}$
- Suppose $q>0$, $V_{ab}>0$
	- \triangleright This would be what happens, e.g., for resistor
		- The charge "falls" to a lower potential energy

$\triangleright \Delta U < 0$

• What happened to the energy?

17 \triangleright In the mechanical analogue of a falling mass, the loss of potential energy is compensated by an increase in kinetic energy

- In the electric case we know that the charges are not really accelerated
	- \triangleright Because they collide with the atoms of the material and get scattered
	- \triangleright All we get is a very slow drift
	- \triangleright Also, we know that the current (= flow of charge) into the element is equal to the current out of the element
		- This could not happen if there was a net acceleration
- The energy is transferred from the charges to the atoms of the material in the collisions
- The atoms vibrate more violently \rightarrow the material heats up.
	- \triangleright Principle of toaster oven, electric space heater, lightbulb

- Could also have $V_b > V_a$ \triangleright e.g., in a source of emf
- Then the change of potential energy is positive
	- \triangleright the element delivers electrical energy to the system
- The amount of energy delivered to the system or delivered by the system is always q $|V_{ab}|$
	- \triangleright where q is the amount of charge that is moved from one terminal to the other

Power

• Reminder: Power is the rare of energy delivered or absorbed per unit time

• $P = dE/dt$

 \triangleright Units: Joule/second = Watt (W)

- But $E = qV_{ab}$
- $P = V_{ab} dq/dt = V_{ab}I$

Power dissipated as heat in a resistance

 $V_{ab} > 0$

- $P = IV_{ab}$
- But Ohm's law: $I = V_{ab}/R$

$$
P = V_{ab}I = I^2R = \frac{V_{ab}^2}{R}
$$

• Resistors have a "power rating" = the maximum power that can be transferred to them before they get damaged (catch on fire!)

- 1. The 30 W bulb carries the greater current and has the higher resistance
- 2. The 30 W bulb carries the greater current and the 60 W bulb has the higher resistance
- 3. The 30 W bulb has the higher resistance, but the the 60 W bulb carries the greater current
- 22 4. The 60 W bulb carries the greater current and has the higher resistance

Answer

- 3: The 30 W bulb has the higher resistance, but the the 60 W bulb carries the greater current
- The potential difference is the same across the two bulbs. The power delivered is $P = V_{ab}$ I. Then the 60 W bulb with its higher power rating must carry the highest current. But high current flows where the resistance is smallest, so the 60 W bulb must have the smaller resistance

Power output of a source

- $P = V_{ab}$ |
- $V_{ab} = \varepsilon Ir$
- \bullet P = ϵ I 2 r

Energy dissipated by the internal resistance of the source

Power input to a source

- Suppose that the external circuit is itself a source of emf
- For example, the alternator of a car recharging its battery
- Or the charger of your cell phone or notebook or ipod

 \mathcal{E} . r

Battery

External circuit

Problem

• A copper cable needs to carry a current of 300 A with a power loss of < 2 W/m. What is the required radius of the copper cable?

P = 1² R
Want P < P₀ = 2 W (per meter)
→ R (per meter) < P₀/1².
Last time, R of cylindrical wire, length L, radius r
R = ρ L/(π r²)
→ ρ/(π r²) < P₀/1²

$$
r > I \sqrt{\frac{\rho}{\pi P_0}}
$$
 = 200 $\sqrt{\frac{1.7 \cdot 10^{-8}}{\pi 2}}$ = 1.6 cm