


# Fall 2004 Physics 3 Tu-Th Section

Claudio Campagnari  
Lecture 16: 22 Nov. 2004


Web page:  
<http://hep.ucsb.edu/people/claudio/ph3-04/>

# Resistor in parallel or in series


- In parallel:

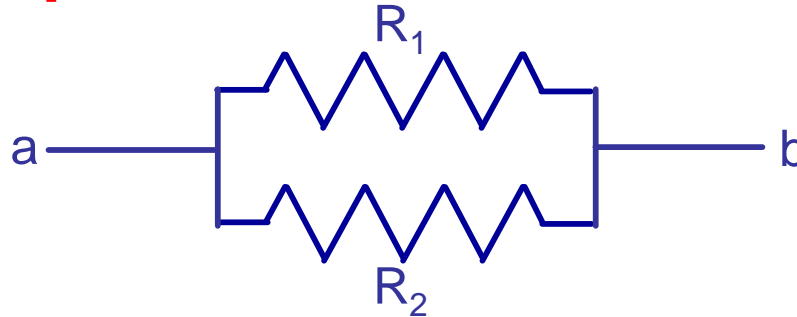

- In series

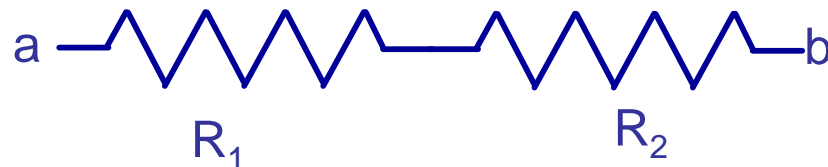


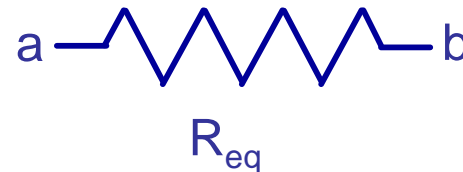- In both cases these pieces of a circuit can be thought of as "equivalent" to a single resistor




- Equivalent means that for a given  $V_{ab}$  the total current flowing would be the same as if it was a single resistor of resistance  $R_{eq}$ , i.e.,  $I = V_{ab}/R$

# $R_{eq}$ for resistors in series

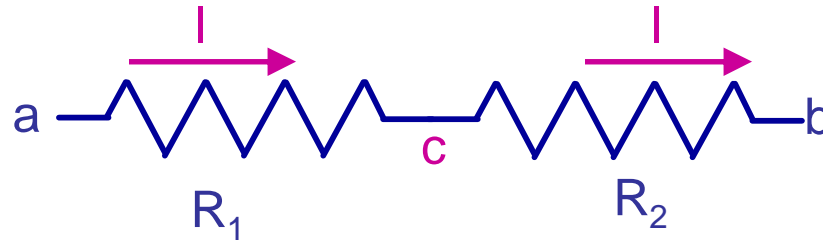

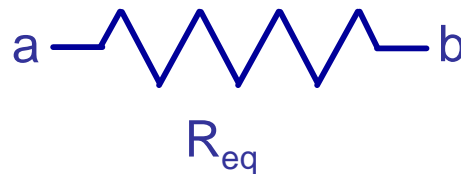- The current flowing through the two resistors is the same
- The voltage drops are
  - $V_{ac} = I R_1$  and  $V_{cb} = I R_2$
  - $V_{ab} = V_a - V_b = V_a - V_c + V_c - V_b = V_{ac} + V_{cb}$
  - $V_{ab} = I R_1 + I R_2 = I (R_1 + R_2)$
- Same as the current flowing through equivalent resistance  $R_{eq} = R_1 + R_2$




$$R_{eq} = R_1 + R_2$$

# Resistors in series, comments


- It makes sense that the resistances add
- Remember, resistance is something that impedes the flow of current
- If the current has to go through both resistors, the current has to overcome two "obstacles" to its flow



# $R_{eq}$ for resistors in parallel

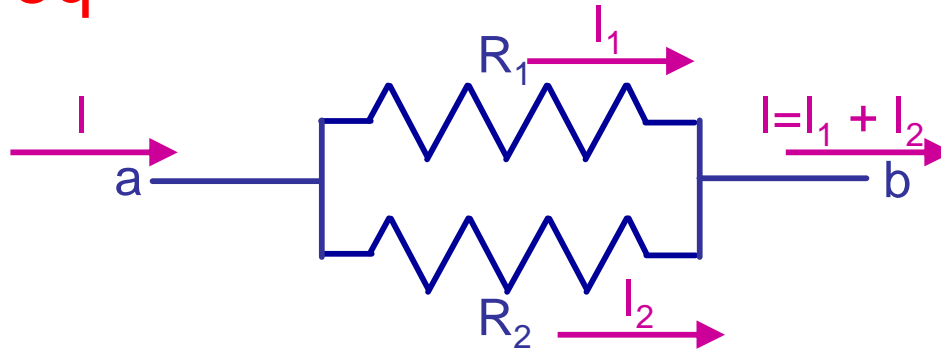


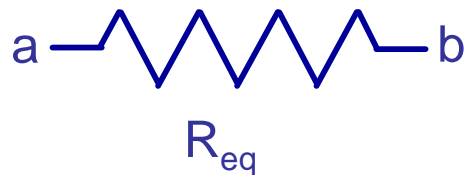- The currents in the two resistors are different
- But the voltage drops across the two resistors are the same
  - $V_{ab} = I_1 R_1 = I_2 R_2$
  - $I = I_1 + I_2 = V_{ab} (1/R_1 + 1/R_2)$
- Same as the current flowing through equivalent resistance  $R_{eq}$



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$
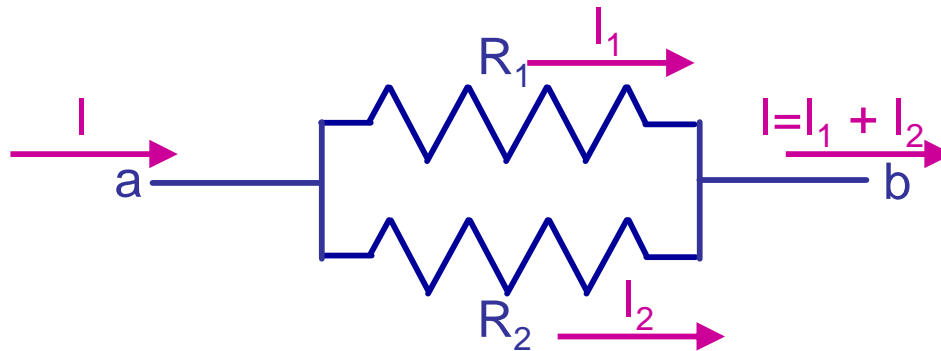
# How does the current split between two resistors in parallel?




- $V_{ab} = I_1 R_1 = I_2 R_2 \rightarrow \frac{I_1}{I_2} = \frac{R_2}{R_1}$
- The current wants to flow through the smaller resistor
  - Makes sense!
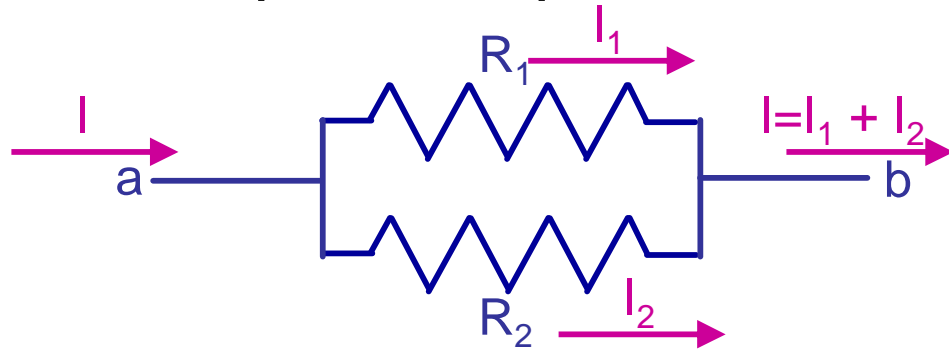
# Resistors in parallel, comments

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

- $R_{eq}$  is always  $< R_1$  and  $< R_2$
- This also makes sense
- When the current encounters two resistors in parallel, there are two possible paths for the current to flow



- It makes sense that the current will have an easier time going past the "obstacle" than it would have if only one resistance was present

# Summary and contrast with capacitors

Resistors in series:

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

Resistors in parallel:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


Capacitors in series:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

Capacitors in parallel:


$$C_{eq} = C_1 + C_2 + C_3 + \dots$$

# A big resistor and a small resistor...

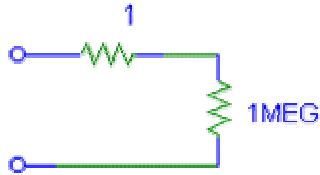

$$R_{eq} = 1 \Omega + 1 \text{ M}\Omega = 1,000,001 \Omega$$

The big resistor wins.....

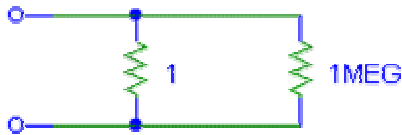


$$\frac{1}{R_{eq}} = \frac{1}{1\Omega} + \frac{1}{1\text{M}\Omega}$$

$$R_{eq} = 0.999999 \Omega$$


The small resistor wins.....

# Find the equivalent resistance

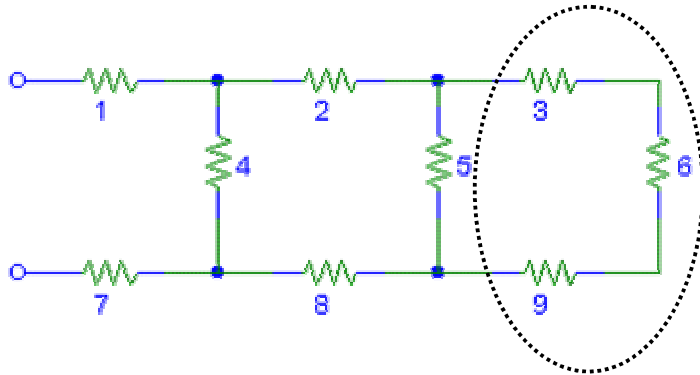

These three are in series.


$$R = 3 + 6 + 9 = 18 \Omega$$

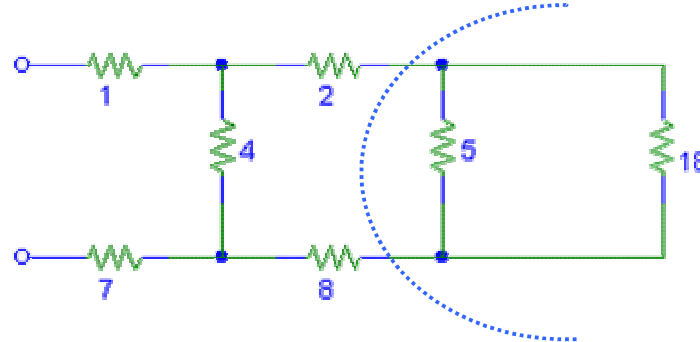

These two are in parallel


$$\frac{1}{R} = \frac{1}{5\Omega} + \frac{1}{18\Omega}$$

$$R = 3.9 \Omega$$

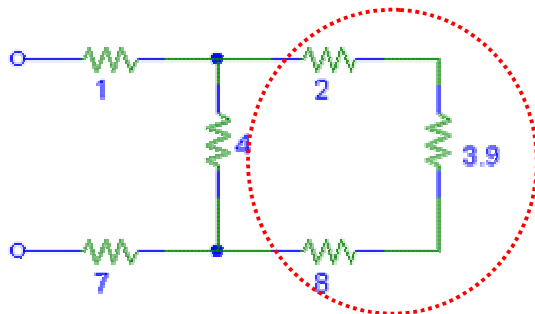

These three are in series


$$R + 2 + 3.9 + 8 = 13.9 \Omega$$

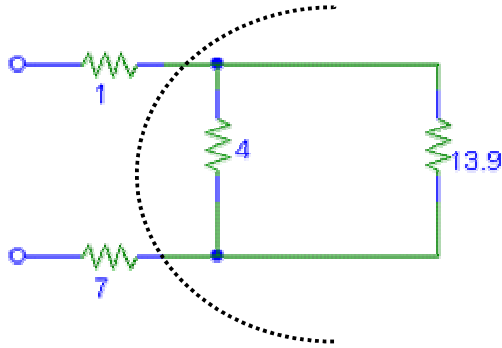


These two are in parallel

$$\frac{1}{R} = \frac{1}{4\Omega} + \frac{1}{13.9\Omega}$$

$$R = 3.1 \Omega$$

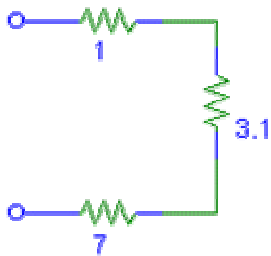

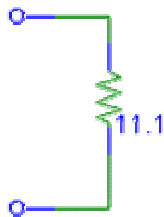
Three resistors in series  
 $R = 1 + 3.1 + 7 = 11.1 \Omega$



$$R_{eq} = 11.1 \Omega$$

Note – for two resistances in parallel,  
 $R_{eq} <$  than each individual one.  
 For two resistances in series,  $R_{eq}$  is greater

# Another example

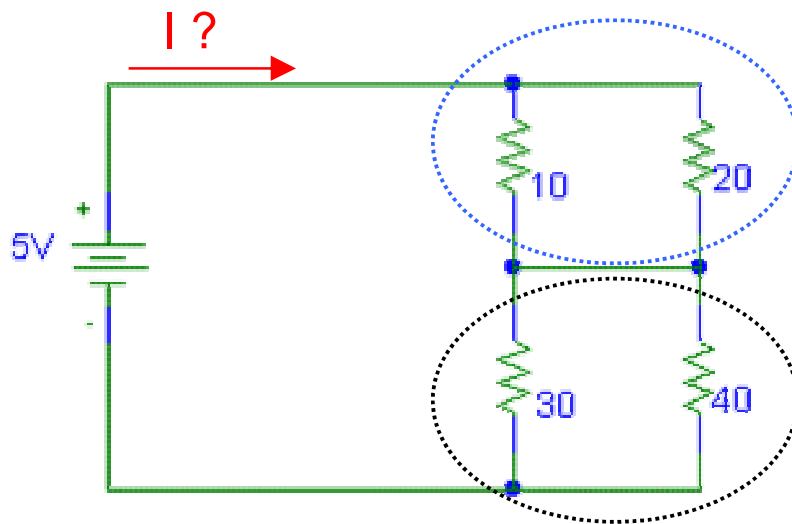


In parallel:

$$\frac{1}{R} = \frac{1}{10\Omega} + \frac{1}{20\Omega}$$
$$R = 6.67\Omega$$

In parallel:

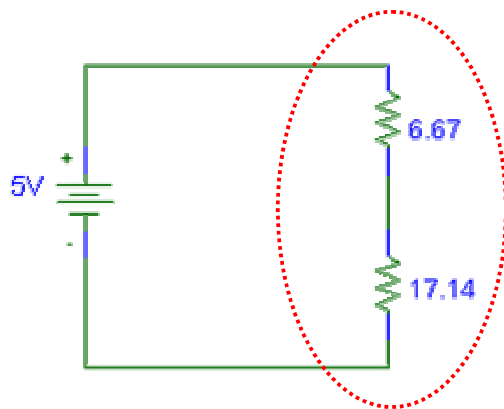
$$\frac{1}{R} = \frac{1}{30\Omega} + \frac{1}{40\Omega}$$
$$R = 17.14\Omega$$



In series:

$$R = 6.67 + 17.14$$

$$R = 23.81\Omega$$

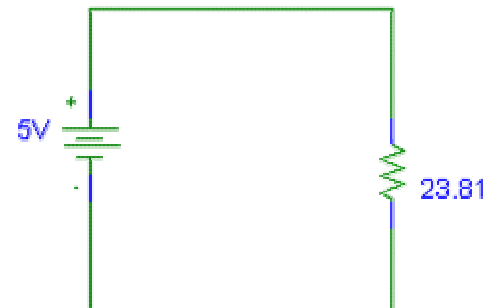


$$I = \frac{V}{R}$$

$$I = \frac{5\text{ V}}{23.81\Omega} = 0.21\text{ A}$$



# Another example (k means $k\Omega$ )


"Short",  $R=0$

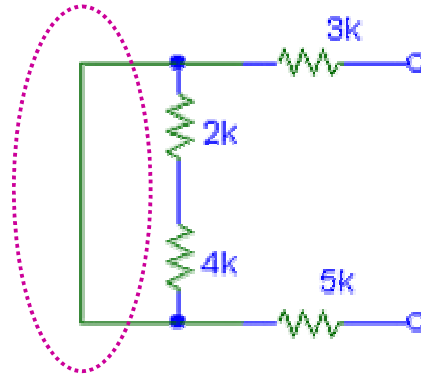

$$\text{Series: } R = 3 + 5 = 8 \text{ k}\Omega$$
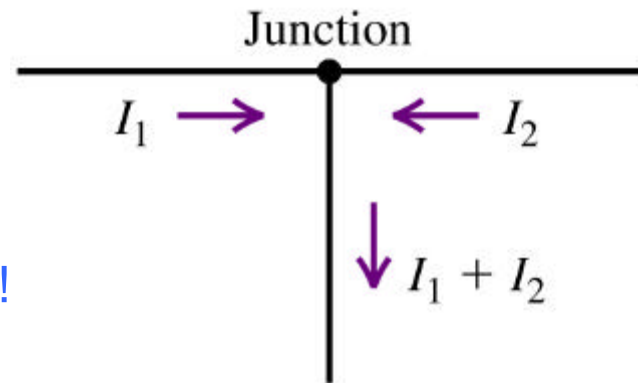
# Kirchoff's rules

- We have already applied them, at least implicitly
- First rule: at a node (or junction)  $\Sigma I = 0$




Careful about the signs!  
It is a good idea to always draw the arrows!

- This is basically a statement that charge is conserved
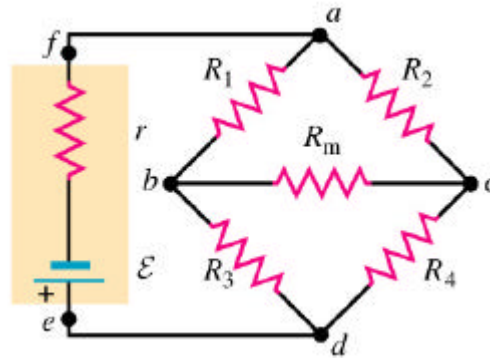
# Kirchoff's rules (continued)

- Second rule: the total voltage drop across a closed loop is zero



For example:

$$V_{ab} + V_{bc} + V_{ca} = 0$$


$$(V_a - V_b) + (V_b - V_c) + (V_c - V_a) = 0$$

But this holds for any loop,


e.g. a-b-d-c-a or b-a-f-e-d-b, .....
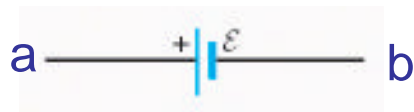
# Careful about signs:

- When you apply Kirchoff's 2<sup>nd</sup> rule, the absolute value of the voltage drop across a resistor is  $IR$  and across a source of emf is  $\varepsilon$
- You must keep the sign straight! For emf, it is easy. For resistors, depends on the sign of  $I$



$$V_{ab} = +\varepsilon$$

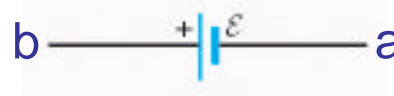

$$V_{ab} = -\varepsilon$$




$$V_{ab} = IR$$



$$V_{ab} = -IR$$


These signs are such that current always runs from high to low potential. Note algebraically  $I$  can be +ve or -ve. What matters is your convention, i.e., the direction of the arrow

# Another example: find $R_{eq}$

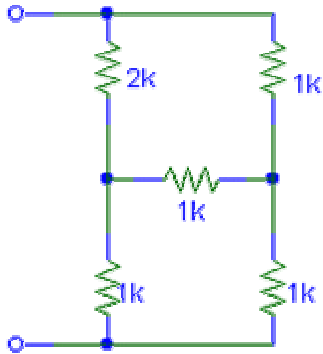

Add a fictitious source of current, say  $I=1A$ , across the terminals. Then if I can calculate the voltage across the terminals,  $R = V/I$ .

Also, label everything!!!!!!

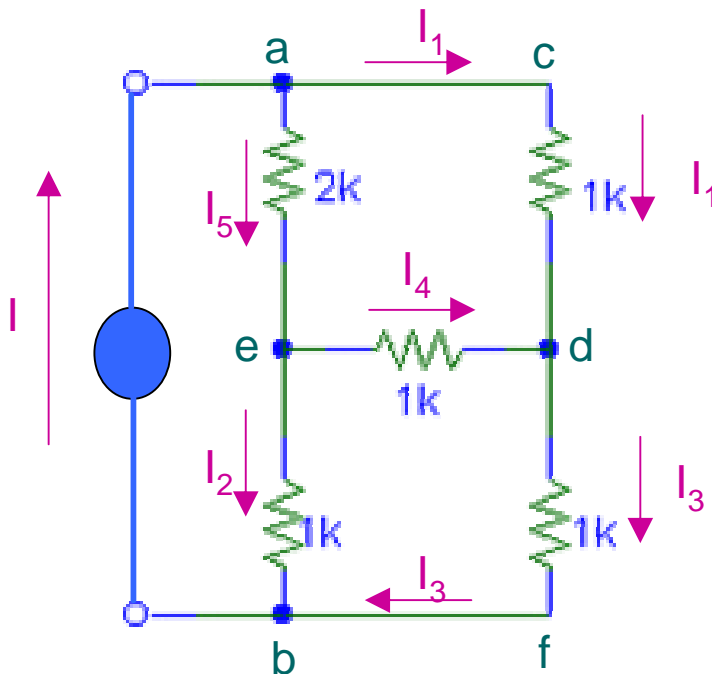

## Kirchoff law for current:

$$\text{Node a: } I = I_1 + I_5$$


$$\text{Node e: } I_5 = I_4 + I_2$$

$$\text{Node d: } I_4 + I_1 = I_3$$

$$\text{Node b: } I_2 + I_3 = I$$

4 equations, 5 unknowns

$(I_1, I_2, I_3, I_4, I_5)$

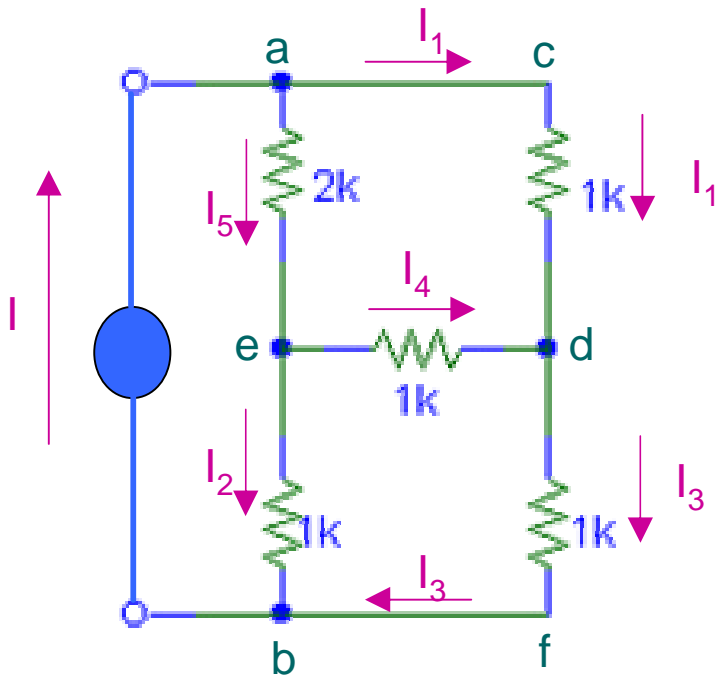

Kirchoff law for current:

- Node a:  $I = I_1 + I_5$
- Node e:  $I_5 = I_4 + I_2$
- Node d:  $I_4 + I_1 = I_3$
- Node b:  $I_2 + I_3 = I$

Now I apply Kirchoff law for voltage loops.  
But let's be smart about it!

I want  $V_{ab}$  (or  $V_{cf}$ , they are the same)

$$V_{ab} = 2I_5 + I_2$$

$$V_{cf} = I_1 + I_3$$

Try to eliminate variables and remain with  $I_5, I_2$

Node b: eliminates  $I_3$ :

$$I_3 = I - I_2$$

Node a: eliminates  $I_1$ :

$$I_1 = I - I_5$$


acdea loop:  $I_1 - I_4 - 2I_5 = 0 \rightarrow I - I_5 - I_4 - 2I_5 = 0 \rightarrow I_4 = I - 3I_5$

Node e:  $I_5 = (I - 3I_5) + I_2 \rightarrow 4I_5 - I_2 = I$

acdfbea loop:  $I_1 + I_3 - I_2 - 2I_5 = 0$

$$(I - I_5) + (I - I_2) - 2I_5 = 0$$

$$2I - 2I_2 - 3I_5 = 0$$

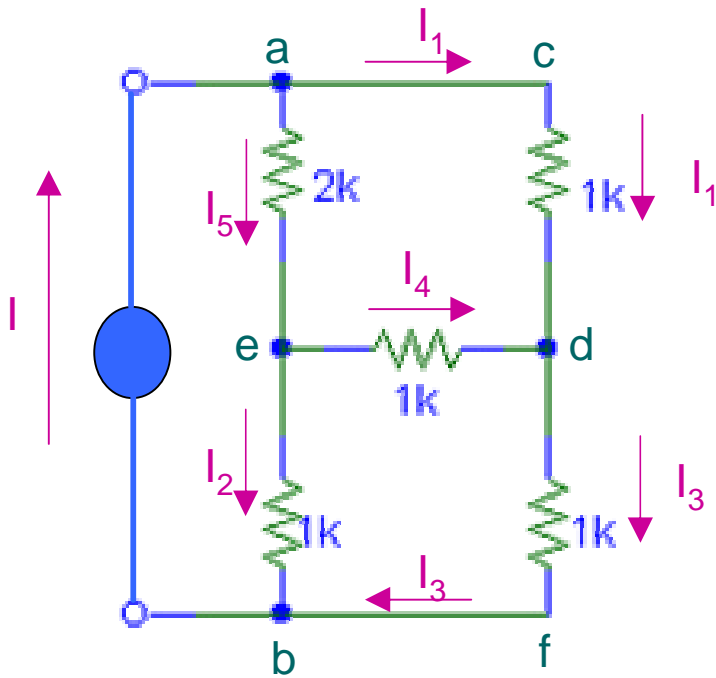

$$4I_5 - I_2 = I$$

$$2I - 2I_2 - 3I_5 = 0$$

Solution:

$$I_2 = 5I/11 \text{ and } I_5 = 4I/11$$

Then:



$$V_{ab} = 2I_5 + I_2$$

$$V_{ab} = 13I/11$$

$$R_{eq} = 13/11 \text{ k}\Omega = 1.2 \text{ k}\Omega$$


Note: Example 26.6 in the textbook is essentially the same.  
 (It has resistances of  $\Omega$  instead of  $k\Omega$ )

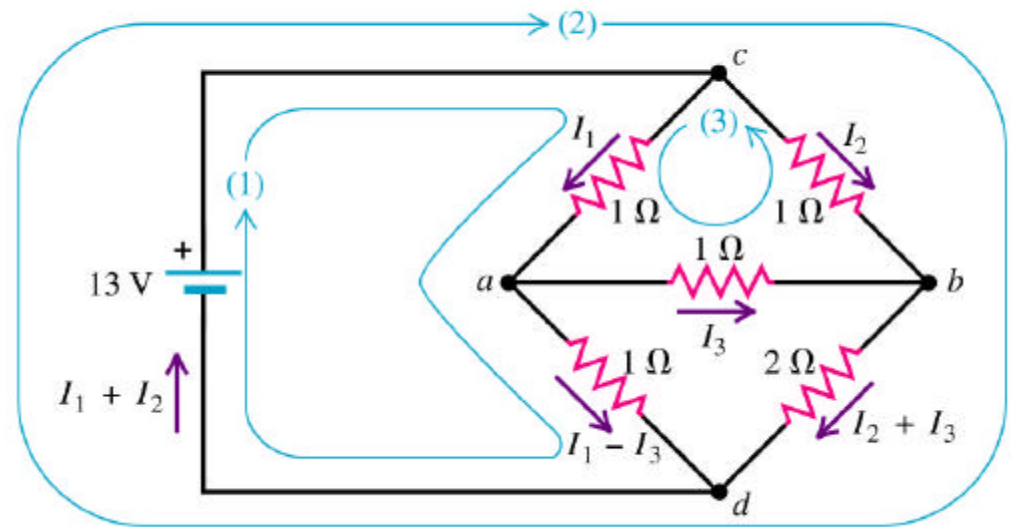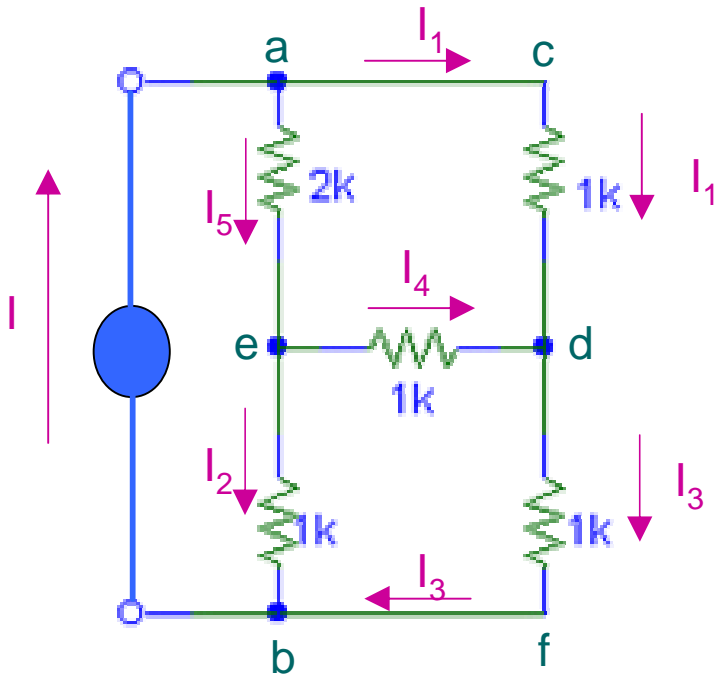The book solves it using a battery rather than a fictitious current source. But the answer is the same, as it should!  
 Check out the alternative method for yourself!






Find  $R_{eq}$  of this circuit:

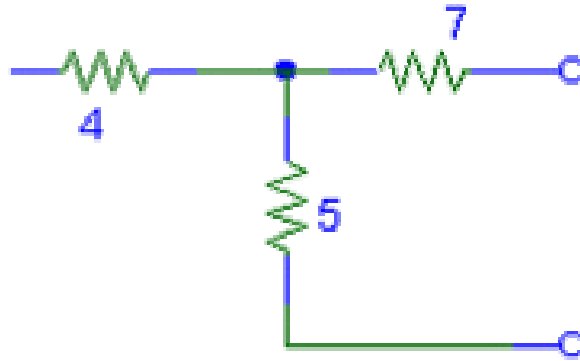


- The other side of the 4 Ω resistor is not connected to anything
- It is as if it was not there!
- Two resistors in series,  $R = 7 \Omega + 5 \Omega = 12 \Omega$


# Another problem.....

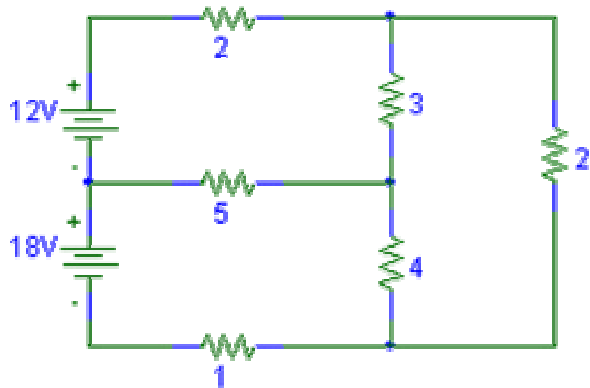

Find the current through the 5  $\Omega$  resistor

First step: Label everything!

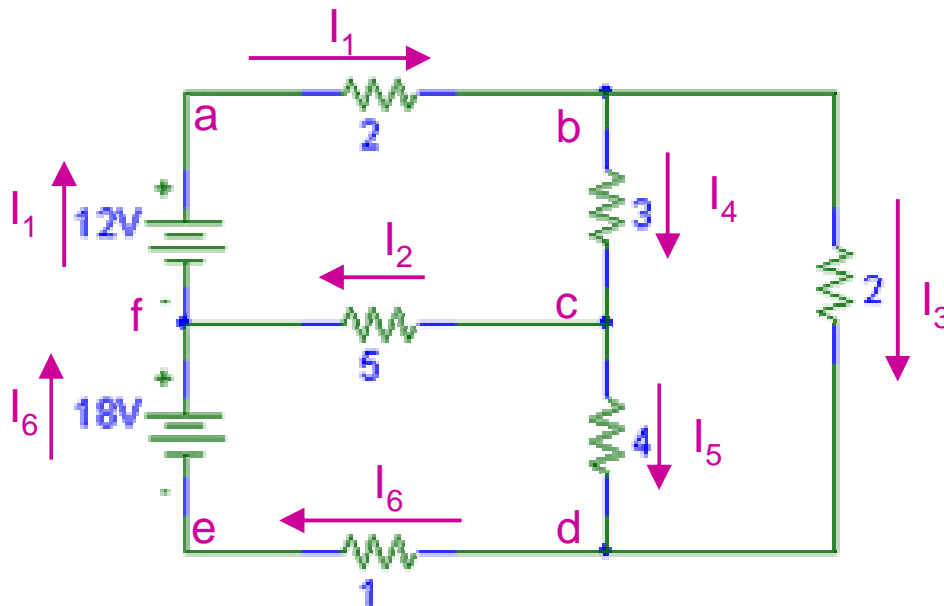

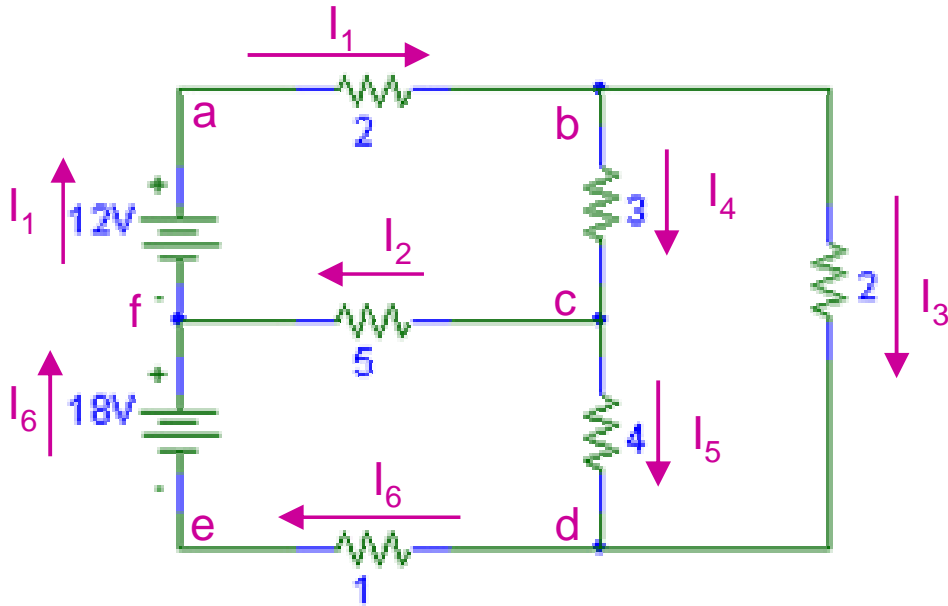

Use Kirchoff law for current nodes to eliminate some variables.

Node c:  $I_4 = I_2 + I_5 \rightarrow$  eliminate  $I_4$

Node d:  $I_6 = I_5 + I_3 \rightarrow$  eliminate  $I_6$

Node b:  $I_1 = I_3 + I_4 = I_3 + I_2 + I_5 \rightarrow$  eliminate  $I_1$

Node f:  $I_6 + I_2 = I_1$


$(I_5 + I_3) + I_2 = I_3 + I_2 + I_5 \rightarrow$  no extra information !

Now everything is in terms of  $I_2$ ,  $I_3$  and  $I_5$

It is easy to eliminate  $I_3$ :

Loop bdb:  $3I_4 + 4I_5 - 2I_3 = 0$

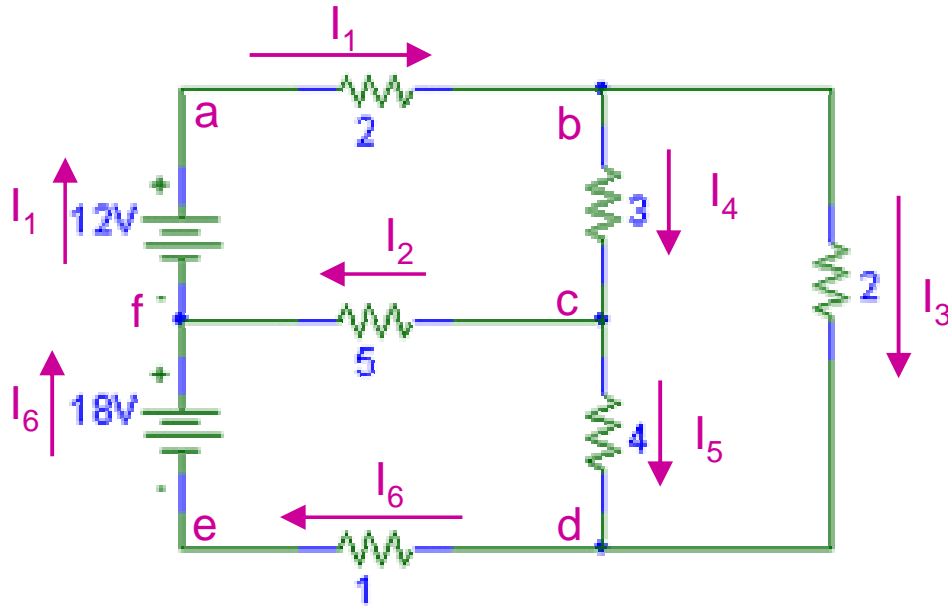$3(I_2 + I_5) + 4I_5 - 2I_3 = 0 \rightarrow I_3 = \frac{1}{2} (3I_2 + 7I_5)$



All currents in terms of  $I_2$  and  $I_5$ :

$$I_1 = \frac{1}{2} (5I_2 + 9I_5)$$

$$I_3 = \frac{1}{2} (3I_2 + 7I_5)$$

$$I_4 = I_2 + I_5$$

$$I_6 = \frac{1}{2} (3I_2 + 9I_5)$$

Loop fabcf:

$$-12 + 2I_1 + 3I_4 - 5I_2 = 0$$

$$-12 + 5I_2 + 9I_5 + 3I_2 + 3I_5 - 5I_2 = 0$$

$$12I_5 + 3I_2 = 12$$

Loop fcdef

$$-5I_2 + 4I_5 + I_6 - 18 = 0$$

$$-5I_2 + 4I_5 + \frac{3}{2} I_2 + \frac{9}{2} I_2 - 18 = 0$$

$$13I_5 - 7I_2 = 36$$

Two equations, two unknowns, can solve, get  $I_2 = -2.24 \text{ A}$