4/7

(15) 3.

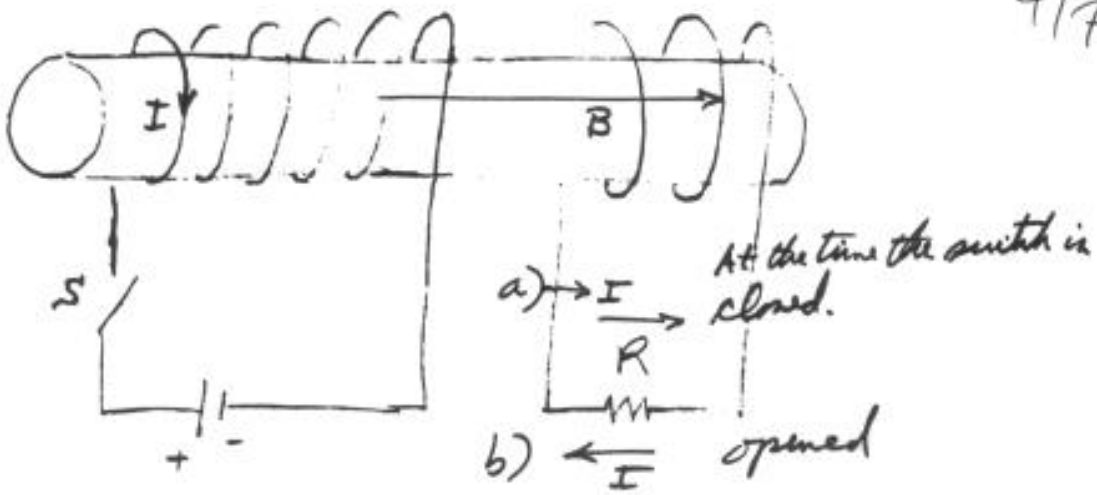

What is the direction of the current through the resistor R when S is

a) closed? left to right $\longrightarrow$

b) opened? right to left $\longleftarrow$